

CART 360

ETUDE THREE: Loopy-Looper

ZAHRA AHMADI

STUDENT ID: 40047185

Links:

<https://a-zahra.github.io/Cart-360/Website/index.html>

<https://github.com/A-Zahra/Cart-360/tree/master/Etudes>

## PART ONE: BASIC ANALOG TONE CREATION

On this circuit, first, I had 10 k $\Omega$  resistors for both the buttons and the RGB LED. Through running my code to the Arduino, I found that my RGB LED is not being turned on. I changed my resistors to 200  $\Omega$  resistors and again it did not turn on. After ensuring that my code is working properly, I realized that I might have burnt my LED by using 10 k $\Omega$  resistors. This time, I kept the 200  $\Omega$  resistors and I changed my RGB LED. The RGB LED turned on. Therefore, I learned that 10 k $\Omega$  resistors are not appropriate for the RGB LED, since their resistance against the voltage is not adequate and thereby, the LED is receiving a rate of current which is more than what the LED can bear. This is why the LED burnt.



